

Two Port Networks- Transmission-Parameter, h-Parameter	
Name: Dheerendra Amrute	Experiment No.: 07
Roll Number: 23EE019	Date: 18-11-2024

Aim:


To verify the Two port Network Transmission Parameters and Hybrid parameters.

Theoretical Calculation:

Que 1. Calculate the h parameters of the given network.

Experiment - 7 60 Two port Network

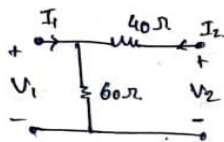Que 1 Calculate h parameter of the given Network



or h parameters:

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$V_1 = 60(I_1 + I_2)$$

$$V_1 = 60I_1 + 60I_2 \quad \text{--- (1)}$$

$$V_2 = 40I_2 + 60(I_1 + I_2)$$

$$V_2 = 40I_2 + 60I_1 + 60I_2$$

$$V_2 = 60I_1 + 100I_2 \quad \text{--- (2)}$$

from (1) $I_2 = \frac{V_1 - 60I_1}{60}$

$$I_2 = \frac{-60I_1 + V_2}{100} = \frac{V_2 - 60I_1}{100}$$

$$V_2 = 60I_1 + 60 \left(\frac{V_2 - 60I_1}{100} \right)$$

$$V_1 = 60I_1 + \frac{6V_2 - 360I_1}{10}$$

$$V_1 = 24I_1 + \frac{6V_2}{10}$$

$$\boxed{V_1 = 24I_1 + 0.6V_2} \quad \text{--- (3)}$$

$$V_2 = 60I_1 + 100I_2$$

$$I_2 = \frac{(60I_1 - V_2)}{100}$$

$$I_2 = \frac{60}{100} I_1 - \frac{V_2}{100}$$

$$\boxed{I_2 = 0.6I_1 - 0.01V_2} \quad \text{--- (4)}$$

Putting I_2 in eq (2)

$$V_2 = 60I_1 - 100 \left(\frac{V_1 - 60I_1}{60} \right)$$

$$V_2 = 60I_1 - \frac{100V_1}{60} + 1000I_1$$

$$V_2 = 1060I_1 - \frac{100}{60} V_1$$

$$\frac{100}{6} V_1 = 1060I_1 - V_2$$

$$V_1 = \frac{1060 \times 6}{100} I_1 - \frac{6}{100} V_2$$

$$V_1 = 63.6 - 0.06V_2$$

$$V_1 =$$

$$I_2 = \frac{V_1 - 60I_2}{60} \quad \text{--- (from 1)}$$

$$V_2 = 60I_1 + 100I_2 \quad 0.01, 0.6$$


from eq (3) and (4)

$$[h] = \begin{bmatrix} 24 \Omega & 0.6 \\ 0.6 & 0.01 S \end{bmatrix}$$


$$[h] = \begin{bmatrix} 24 \Omega & 0.6 \\ 0.6 & 0.01 S \end{bmatrix}$$

Que 2. Calculate the h parameters of the given network.


Que 2

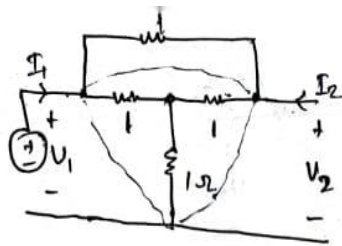

2

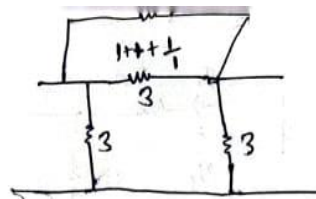

$\frac{1 \times 3}{4}$

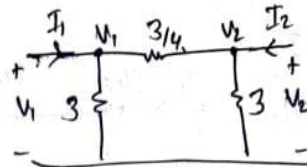

* $\rightarrow \Delta \Rightarrow R_1 + R_2 + \frac{R_1 R_2}{R_3}$

KCL at V_1

$$I_1 + \frac{V_1}{3} = \frac{V_1 - V_2}{3/4}$$

$$I_1 = \frac{V_1}{3} + \frac{4V_1 - 4V_2}{3}$$

$$I_1 = \frac{5V_1 - 4V_2}{3}$$

$$\frac{5V_1}{3} = I_1 + \frac{4}{3}V_2$$

$$V_1 = \frac{3}{5}I_1 + \frac{4}{5}V_2$$

$$V_1 = \frac{3}{5}I_1 + \frac{4}{5}V_2$$

KCL at

$$I_2 = \frac{5}{3}V_2 - \frac{4}{3}I_1 + \frac{16}{15}V_2$$

$$I_2 = -\frac{4}{3}I_1 + \frac{5 \times 16}{15}V_2$$

$$I_2 = -\frac{4}{3}I_1 + \frac{8}{3}V_2$$

$$h = \begin{bmatrix} 0.6 & 0.8 \\ -0.8 & 0.6 \end{bmatrix}$$

For h Parameter

$$V_1 = h_{11}I_1 + h_{12}I_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

KCL at V_2

$$I_2 = \frac{V_2}{3} + \frac{(V_2 - V_1)4}{3}$$

$$I_2 = \frac{V_2 + 4V_2 - 4V_1}{3}$$

$$I_2 = \frac{5}{3}V_2 - \frac{4}{3}V_1$$

$$I_2 = \frac{5}{3}V_2 - \left(\frac{3}{5}I_1 + \frac{4}{5}V_2\right)\frac{4}{3}$$


$$I_2 = \frac{5}{3}V_2 - \frac{3}{5}I_1 - \frac{4}{5}V_2$$

$$I_2 = \left(\frac{5}{3} - \frac{4}{5}\right)V_2 - \frac{3}{5}I_1$$

$$\frac{20 - 12}{15} =$$


Que 3. Calculate the T parameters of the given network.

Que 3

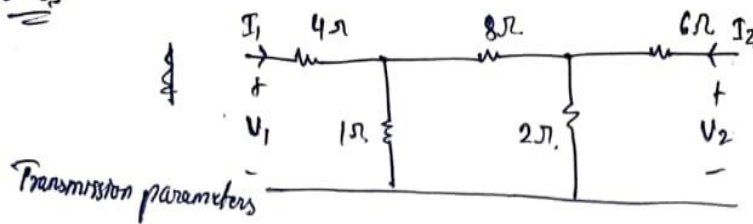

$$V_1 = AV_2 - BI_2$$


$$I_2 = CV_2 - DI_2$$

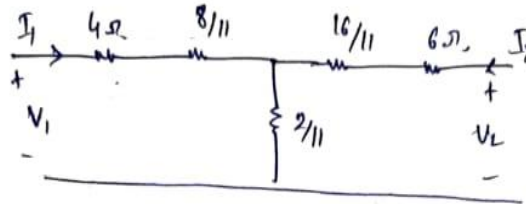

$$V_2 = \frac{84}{11} I_2 + \frac{2}{11} I_1$$

$$\frac{2}{11} I_1 = V_2 - \frac{84}{11} I_2$$

$$I_1 = \frac{11}{2} V_2 - 42 I_2$$

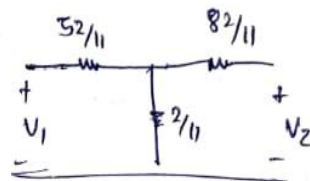

$$[T] = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$V_1 = \frac{54}{11} I_1 + \frac{2}{11} I_2$$



$$V_1 = \frac{54}{11} \left(\frac{11}{2} V_2 - 42 I_2 \right) + \frac{2}{11} I_2 \quad [T] = \begin{bmatrix} 27 & -206 \\ 5.5 & -42 \end{bmatrix}$$

$$V_1 = 27 V_2 - 206 I_2$$

$$I_1 = 5.5 V_2 - 42 I_2$$

Que 4. Calculate the T parameters of the given network.

Que 4

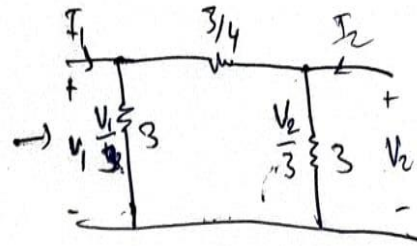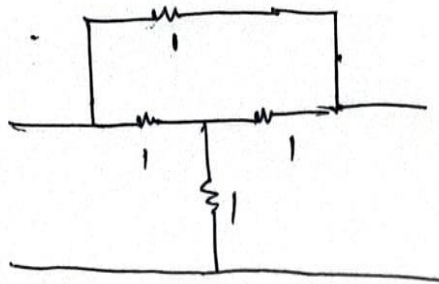

$$\Rightarrow \frac{3}{4} \left(I_2 - \frac{V_2}{3} \right) + V_1 = V_2$$

$$I_1 = - \left(I_2 - \frac{V_2}{3} \right) + \frac{V_1}{3}$$

$$\Rightarrow V_1 = V_2 - \frac{3}{4} I_2 + \frac{1}{4} V_2$$

$$I_1 = - \left(I_2 \right) + \frac{V_2}{3} + 1.25 V_2 - 0.25 I_2$$

$$V_1 = 1.25 V_2 - 0.75 I_2$$


$$I_1 = - \frac{3}{4} V_2 - \frac{5}{4} I_2$$

$$[T] = \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$\Rightarrow [T] = \begin{bmatrix} 1.25 & 0.75 \Omega \\ 0.75 S & 1.25 \end{bmatrix}$$


Que 5. Calculate the h parameters of the given network.

Que 5

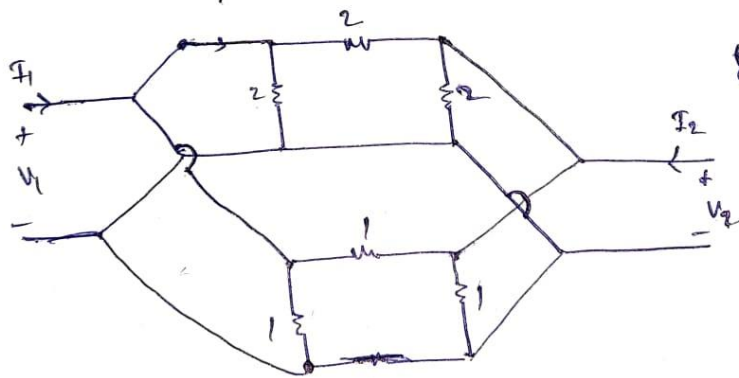

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

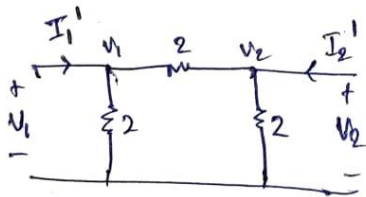

$$I_1' = \frac{V_1 - V_2}{2} + \frac{V_1}{2}$$

$$I_1' = \frac{V_1 - V_2 + V_1}{2}$$

$$I_1' = \frac{2V_1 - V_2}{2}$$


$$I_1' = V_1 - \frac{1}{2} V_2$$

$$I_2' = \frac{V_2}{2} + \frac{V_2 - V_1}{2}$$

$$I_2' = V_2 - \frac{1}{2} V_1$$

$$I_2' = -\frac{1}{2} V_1 + V_2$$
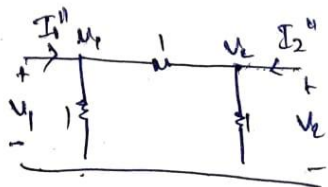
$$[Y_a] = \begin{bmatrix} 1 & -1/2 \\ -1/2 & 1 \end{bmatrix}$$



$$[y_b] = \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix}$$

$$I_1'' = \frac{V_1}{1} + \frac{V_1 - V_2}{1}$$

$$I_1'' = V_1 + V_1 - V_2$$

$$I_1'' = 2V_1 - V_2$$

$$I_2'' = \frac{V_2}{1} + \frac{V_2 - V_1}{1}$$

$$I_2'' = -V_1 + 2V_2$$

$$[y] = [y_a] + [y_b]$$

$$= \begin{bmatrix} 2 & -1 \\ -1 & 2 \end{bmatrix} + \begin{bmatrix} 1 & -1/2 \\ -1/2 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 3 & -3/2 \\ -3/2 & 3 \end{bmatrix} = [y]$$

$$[y] \rightarrow [z]$$

$$[y] = [z]^{-1}$$

$$z = \begin{bmatrix} 0.444 & 2/9 \\ 2/9 & 4/9 \end{bmatrix}$$

↳

$$h_{11} = \frac{\Delta Z}{Z_{22}} = \frac{0.148}{4/9}$$

$$|Z| = 0.148$$

$$h_{11} = 0.833$$

$$h_{22} = \frac{Z_{12}}{Z_{22}} = \frac{2/9 \times 9/4}{4/9} = \frac{2}{4} = 0.5$$

$$h_{21} = \frac{-Z_{21}}{Z_{22}} = -\frac{2/9 \times 9/4}{4/9} = -\frac{2}{4} = -0.5$$


$$h_{22} = \frac{1}{Z_{22}} = \frac{1}{4/9} = \frac{9}{4} = 2.25$$

$$[h] = \begin{bmatrix} 0.833 & 0.5 \\ -0.5 & 2.25 \end{bmatrix}$$


Verification by Simulation:

Que 1. Calculate h parameters for the given network.

Circuit Diagram:

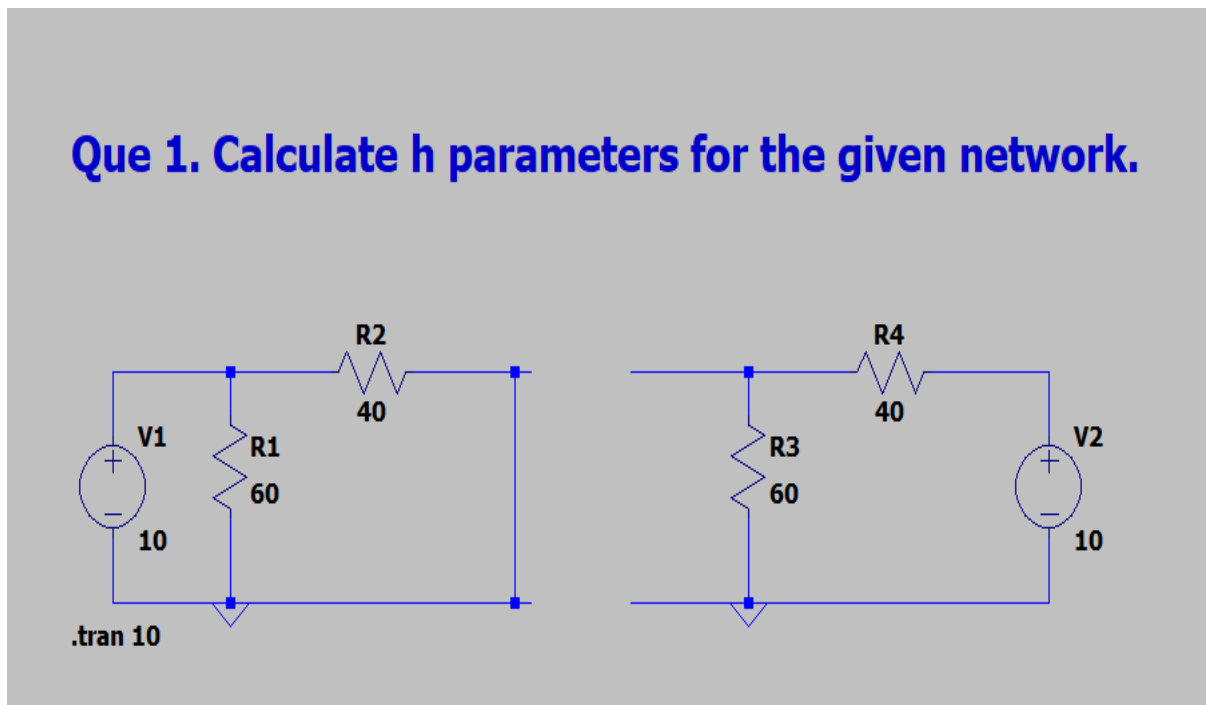

Plot of Voltage/Current:

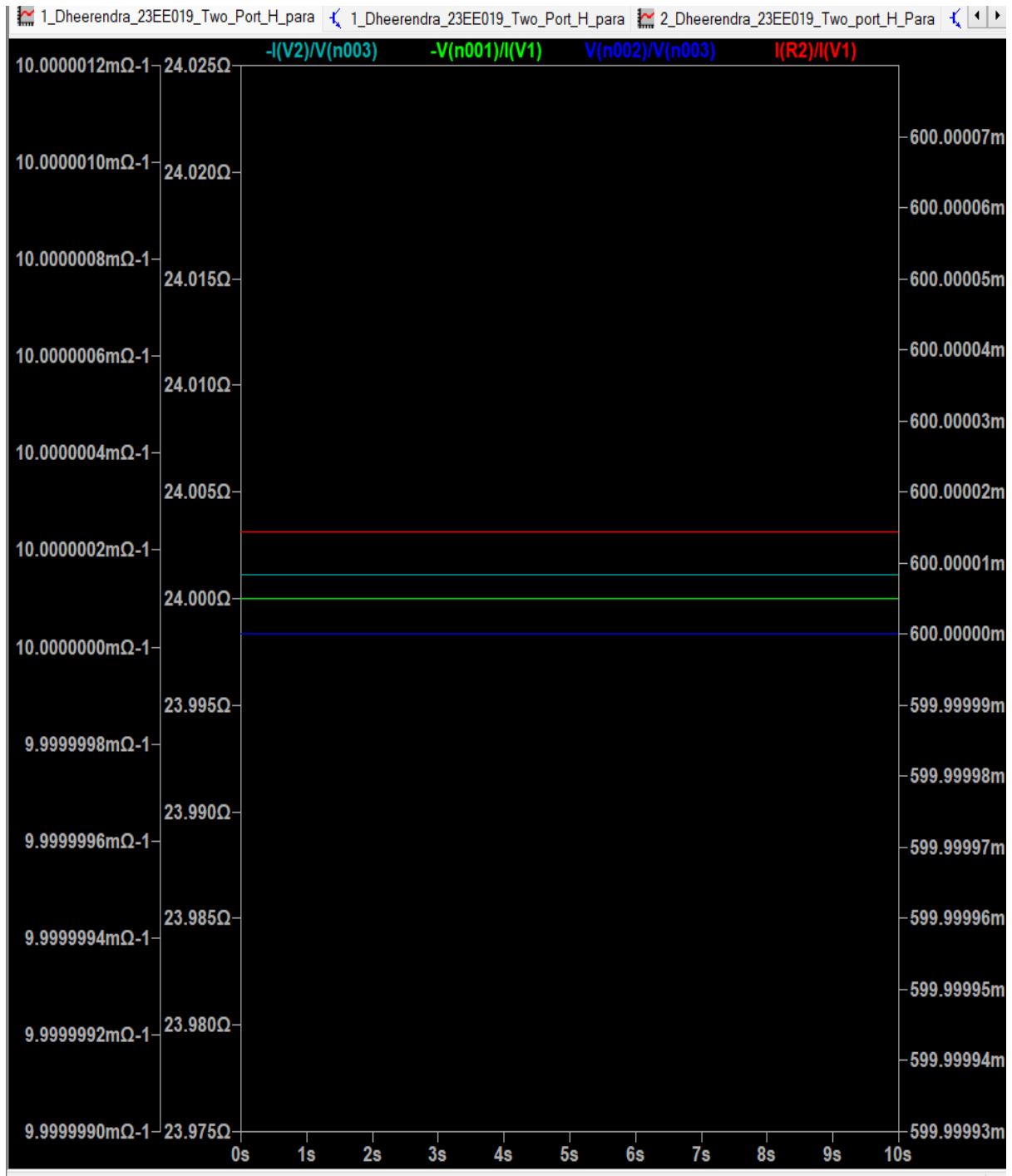


Observation Table:

S. No.	h-Parameters	Theoretical Value	Practical Value
1	h_{11}	24 Ohm	24.000001Ohm
2	h_{12}	0.6	0.6
3	h_{21}	0.6	0.6
4	h_{22}	0.01 Ohm-1	0.01 Ohm-1


Que 2. Calculate the h parameters of the given network.

Circuit Diagram:

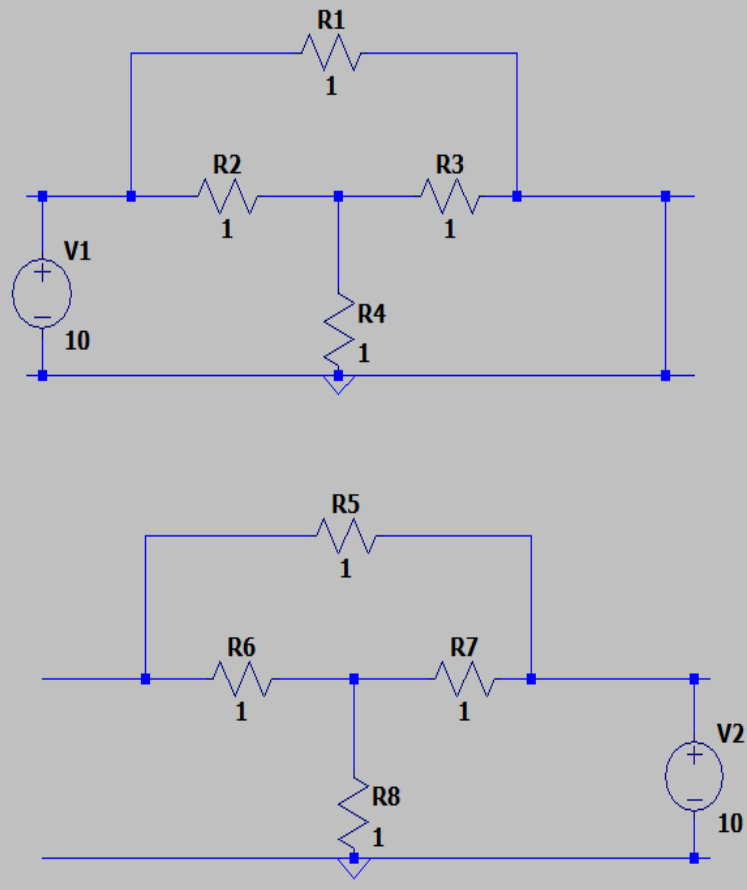Que 2. Calculate the h parameters of the given network.



Plot of Voltage/Current:

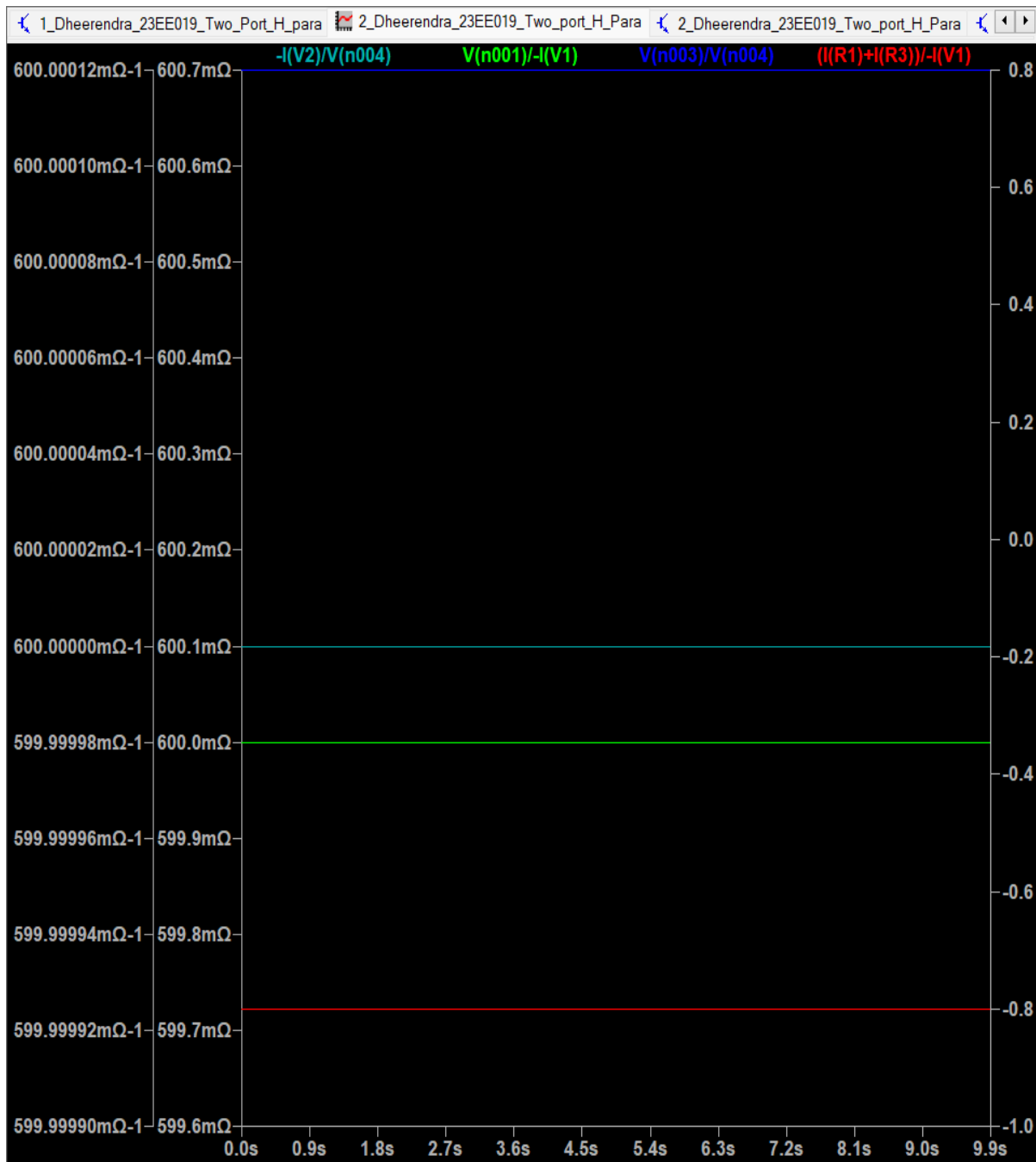


Observation Table:

S. No.	h-Parameters	Theoretical Value	Practical Value
1	h_{11}	0.6 Ohm	0.6 Ohm
2	h_{12}	0.8	0.8
3	h_{21}	-0.8	-0.8
4	h_{22}	0.6 Ohm-1	0.6 Ohm-1

Que 3. Calculate the transmission Parameter for the circuit.

Circuit Diagram:

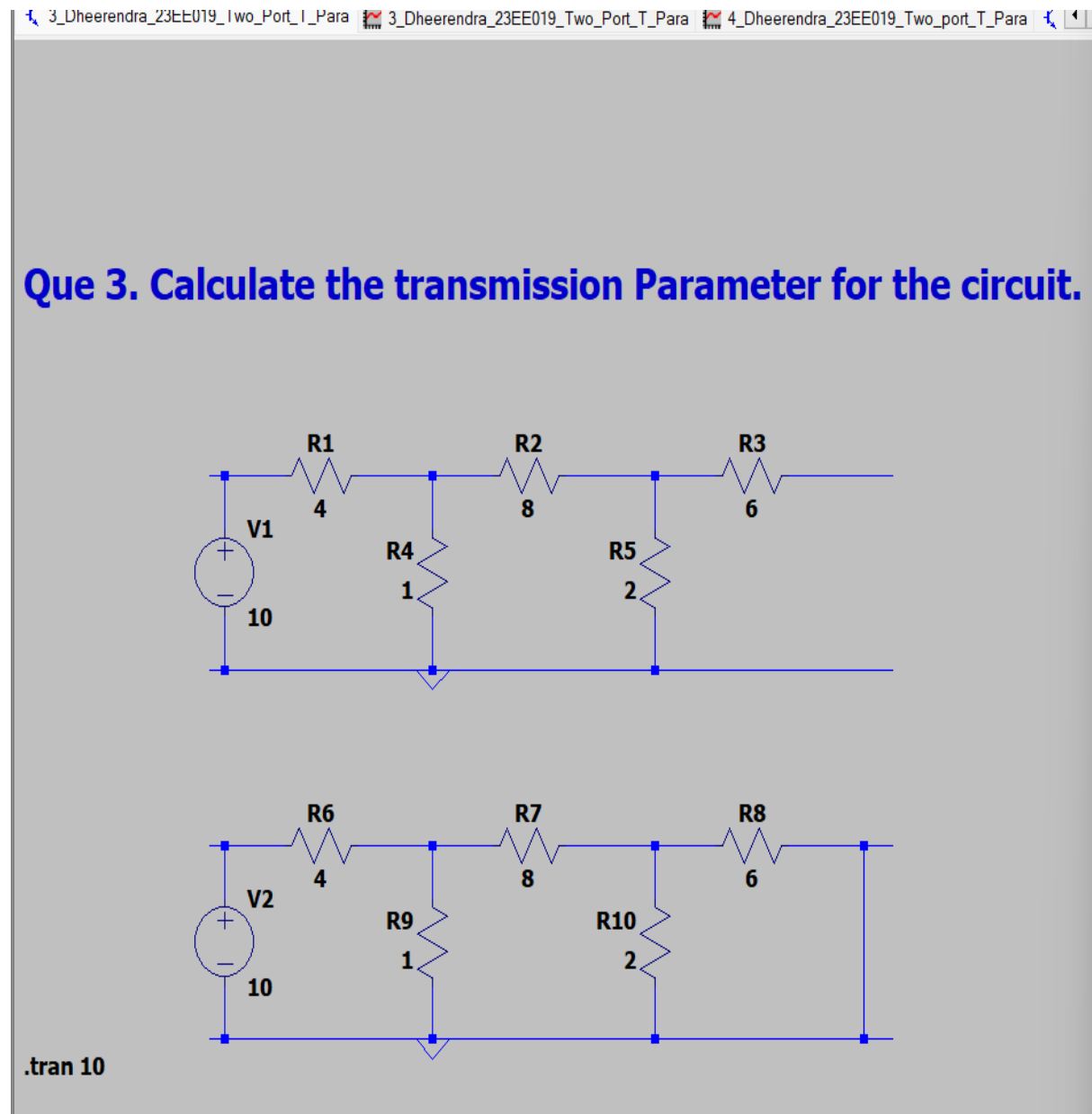

Plot of Voltage/Current:




Observation Table:

S. No.	T-Parameters	Theoretical Value	Practical Value
1	A	27	27.000001
2	B	-206 Ohm	-206.00001Ohm
3	C	5.5 Ohm-1	5.5000004Ohm-1
4	D	-42	-42.000003

Que 4. Calculate the T parameters of the given network.

Circuit Diagram:

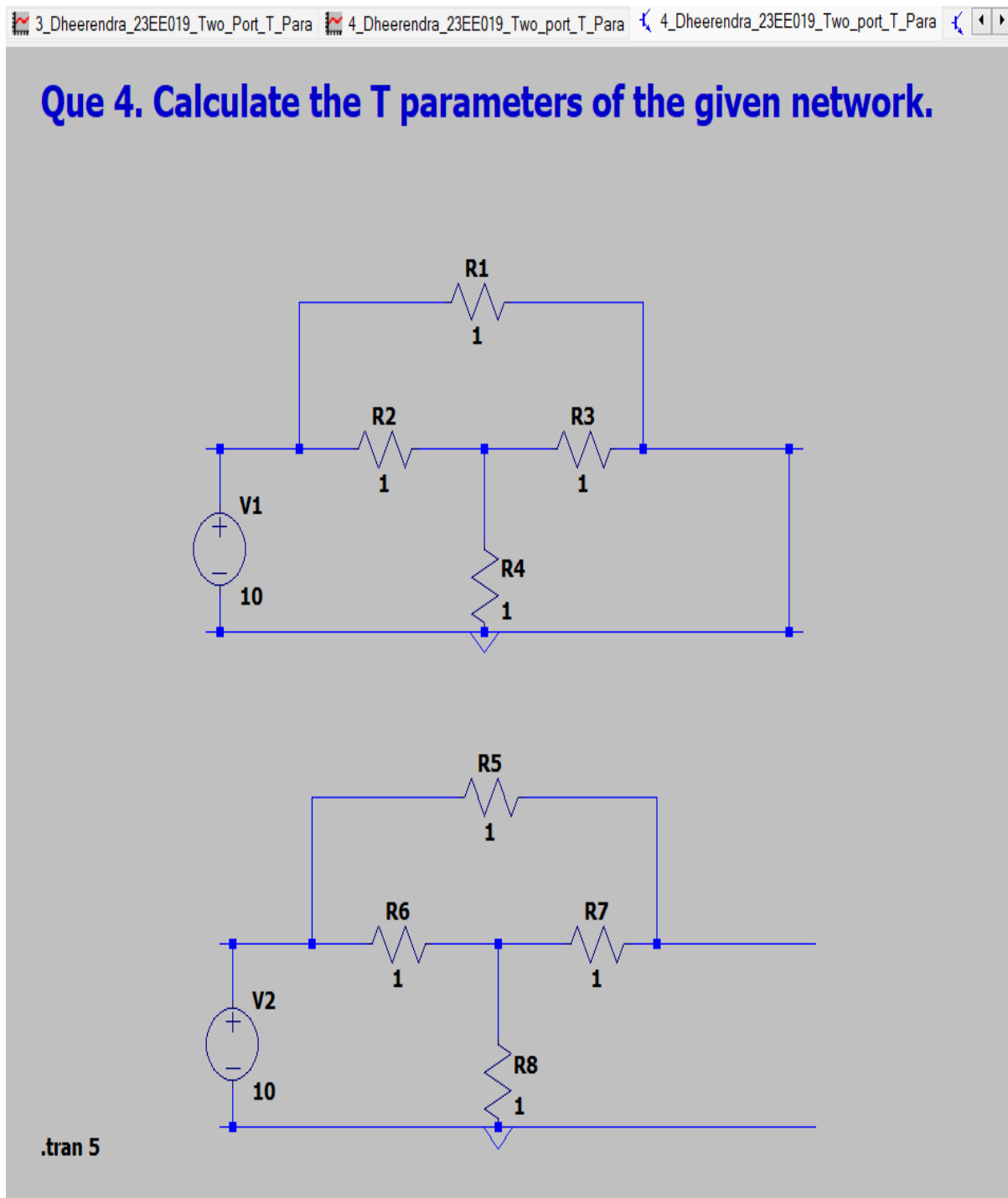

Plot of Voltage/Current:




Observation Table:


S. No.	T-Parameters	Theoretical Value	Practical Value
1	A	1.25	1.25
2	B	0.75 Ohm	750mOhm-1
3	C	0.75 Ohm-1	750mOhm
4	D	1.25	1.25

Que 5. find the H parameter of the given network.

Circuit Diagram:

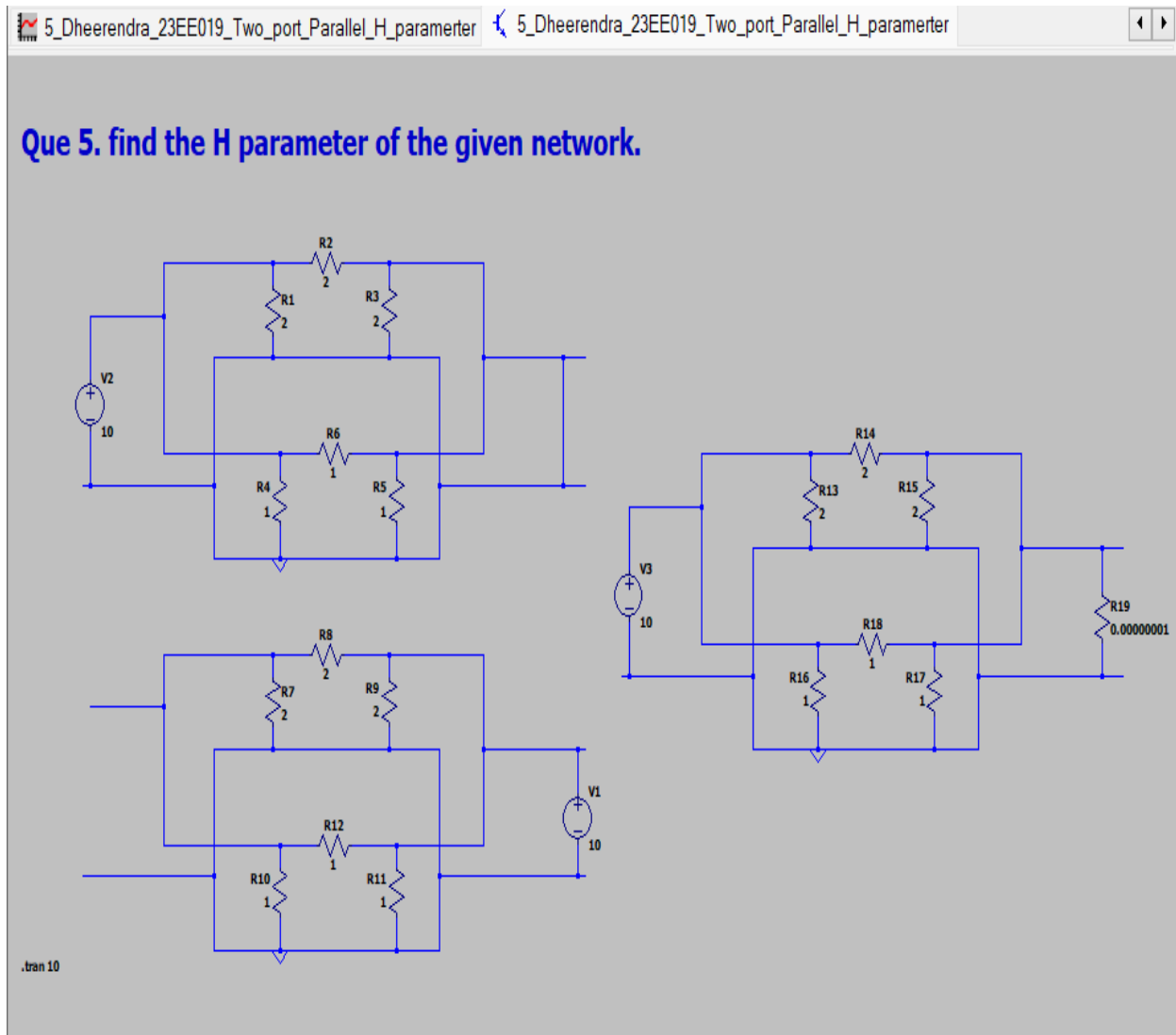

Plot of Voltage/Current:

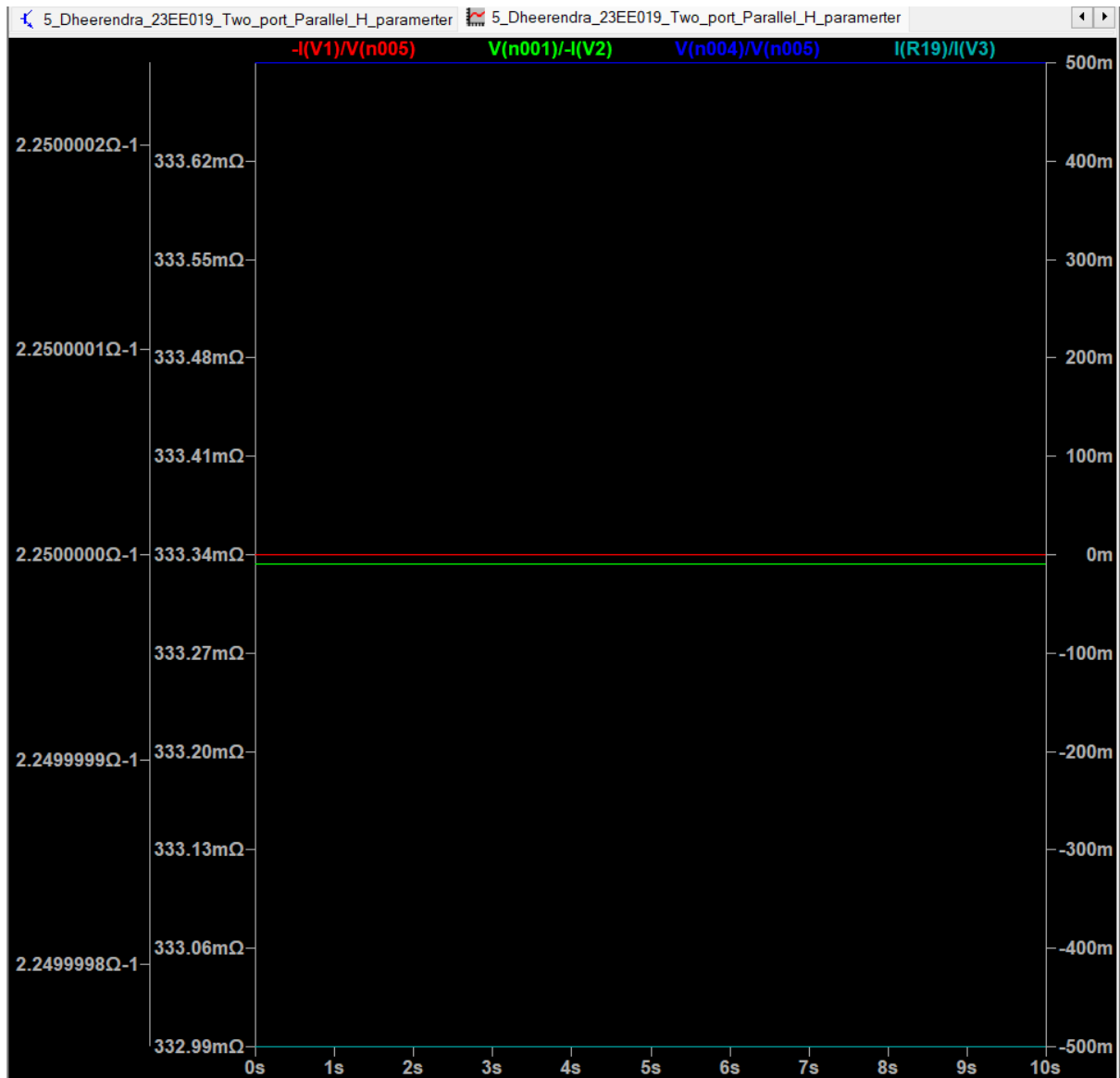

Observation Table:

S. No.	T-Parameters	Theoretical Value	Practical Value
1	A	0.333 Ohm	0.333333 Ohm
2	B	0.5	0.5
3	C	-0.5	-0.5
4	D	2.25 Ohm-1	2.25 Ohm-1

Results and Conclusion:

As we see that the theoretical values of the Transmission parameters and the Hybrid parameters is approximately equal to the practical values of the Transmission parameters and the Hybrid parameters, Hence the Z parameters and Y parameters are Verified.