

Network Synthesis: Foster and Cauer form Realization	
Name: Dheerendra Amrute	Experiment No.: 08
Roll Number: 23EE019	Date: 19-11-2024

Aim:

To Verify the Network Synthesis: Foster and Cauer form Realization

Theoretical Calculation:

Circuit Diagram:

Question 1. Determine the foster I and foster II for the given Impedence.

Ques 1

Foster-I

$$Z(s) = \frac{4(s^2+1)(s^2+16)}{s(s^2+4)} = \frac{A}{s} + \frac{Bs+C}{s^2+4} + Ds$$

$$s=0 \rightarrow \boxed{A=16}$$

$$= \frac{4s^4 + 64s^2 + 4s^2 + 64}{s(s^2+4)} = \frac{4s^4 + 68s^2 + 64}{s(s^2+4)} = 16s^2 + 64 + \frac{Bs^2 + Cs + (Ds^2)(s^2+4)}{s(s^2+4)}$$

$$= 16s^2 + 64 + Bs^2 + Cs + \frac{Ds^4 + 4Ds^2}{s(s^2+4)}$$

$$4s^4 = Ds^4$$

$$\boxed{D=4}$$

$$16s^2 + 64s^2 = 64s^2 + 4s^2$$

$$\Rightarrow (64+4)s^2 = (16+B)s^2$$



$$68-16 = B+4 \times 4 \leftarrow \Rightarrow 68-16 = B+16 \Rightarrow \boxed{B=52}$$

$$52-16 = B$$

$$\boxed{B=36}$$

$$Cs=0 \Rightarrow \boxed{C=0}$$
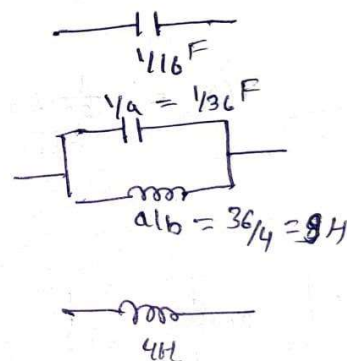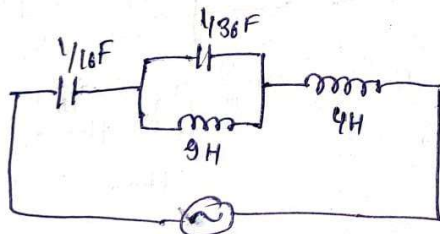
$$Z(s) = \frac{16}{s} + \frac{36s+0}{s^2+4} + 4s$$



Foster - I

$$Z(s) = \frac{4(s^2+1)(s^2+16)}{s(s^2+4)} \Rightarrow Y(s) = \frac{4s(s^2+4)}{4(s^2+1)(s^2+16)}$$

$$Y(s) = \frac{s(s^2+4)}{4(s^2+1)(s^2+16)} = \frac{As+B}{s^2+1} + \frac{Cs+D}{s^2+16}$$

$$\Rightarrow s(s^2+4) = 4[(As+B)(s^2+16) + (Cs+D)(s^2+1)]$$

$$s^3 + 4s = 4[A(s^3 + 16s) + C(s^3 + 1)s + B(s^2 + 16) + D(s^2 + 1)]$$

$$s^3 + 4s = 4[A s^3 + 16As + B s^2 + 16B + C s^3 + Cs + D s^2 + D]$$

$$s^3 = As^3 + Cs^3$$

$$\boxed{\frac{1}{4} = A + C} \quad \text{--- (1)}$$

$$\boxed{A = \frac{1}{5}} \quad C = \frac{4}{5}$$

$$\frac{4s}{4} = 16As + Cs$$



$$\boxed{\frac{1}{4} = 16A + C} \quad \text{--- (2)}$$

$$\boxed{A = \frac{1}{20}}$$


$$\boxed{C = \frac{1}{5}}$$

$$\boxed{B = 0} \quad \boxed{D = 0}$$
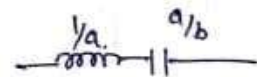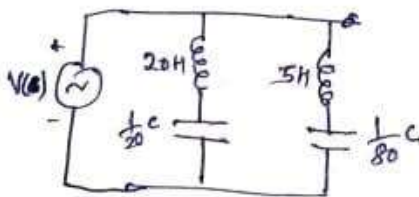
$$Y(s) = \frac{\frac{1}{20}s}{s^2+1} + \frac{\frac{1}{5}s}{s^2+16}$$



the

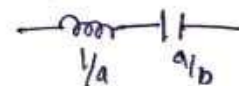

a = 1/20

$$\frac{a}{b} = \frac{\frac{1}{20}}{\frac{1}{1}} = \frac{1}{20}$$


$$\frac{a}{b} = \frac{\frac{1}{5}}{\frac{16}{1}} = \frac{1}{16 \times 5}$$

Question 2 calculate the Cauer I and Cauer II for given Impedance.

Que 2

$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}$$

Cauer-I

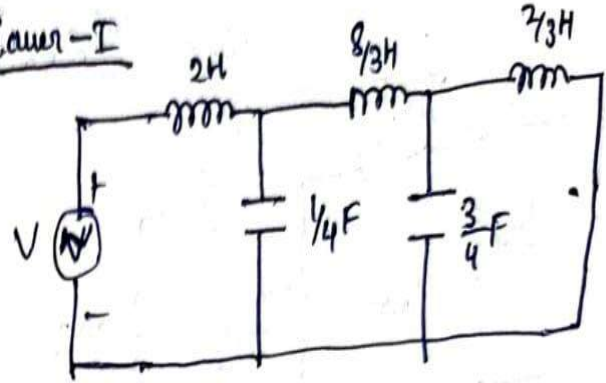

$$s^4 + 4s^2 + 3$$

$$\begin{array}{r} 2s^5 + 12s^3 + 16s \\ 2s^5 + 8s^3 + 6s \\ \hline \end{array} \quad \begin{array}{l} 2s \leftarrow Z(s), L=2H \\ 2s^5 + 8s^3 + 6s \end{array}$$

$$\begin{array}{r} 4s^3 + 10s \\ 4s^3 + 4s^2 + 3 \\ \hline \end{array} \quad \begin{array}{l} \frac{4s}{4} \leftarrow Y(s), C = \frac{1}{4} F \\ s^4 + \frac{10}{4}s^2 \end{array}$$

$$\begin{array}{r} \frac{3}{2}s^2 + 3 \\ 4s^3 + 10s \\ \hline \end{array} \quad \begin{array}{l} s \frac{2}{3} \times 4 \rightarrow \frac{8}{3} \text{ (crossed out)} \\ \frac{3}{2}s^2 + 3 \end{array} \quad \begin{array}{l} \frac{8}{3} \text{ (crossed out)} \\ L = \frac{8}{3} H \end{array}$$

$$\begin{array}{r} \times 2s \\ \frac{3}{2}s^2 + 3 \\ \hline \end{array} \quad \begin{array}{l} \frac{1}{2} \frac{3}{2}s \rightarrow Y(s) \rightarrow \frac{3}{4} F = C \\ \frac{3}{2}s^2 + 3 \end{array}$$

$$\begin{array}{r} 3 \\ 2s \\ \hline 2s \\ \hline \end{array} \quad \begin{array}{l} 2 \times \frac{1}{3} s \rightarrow Z(s) \\ L = \frac{2}{3} H \end{array}$$

Ques 2

Case-2


$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{(s^4 + 4s^2 + 3)} \Rightarrow Y(s) = \frac{s^4 + 4s^2 + 3}{2s^5 + 12s^3 + 16s}$$

$$Y(s) = \frac{3 + 4s^2 + s^4}{16s + 12s^3 + 2s^5}$$

$$\begin{array}{l} 16s + 12s^3 + 2s^5 \overline{) 3 + 4s^2 + s^4} \left(\frac{3}{16s} \rightarrow Y(s) = L = \frac{16}{3} H \right. \\ \underline{3 + \frac{9}{8}s^2 + \frac{3}{8}s^4} \\ \end{array}$$

$$\begin{array}{l} \frac{7}{4}s^2 + \frac{5}{8}s^4 \overline{) 16s + 12s^3 + 2s^5} \left(\frac{4 \times 16}{7s} \rightarrow Z(s) \quad C = \frac{7}{16 \times 4} \right. \\ \underline{16s + \frac{40}{7}s^3} \end{array}$$
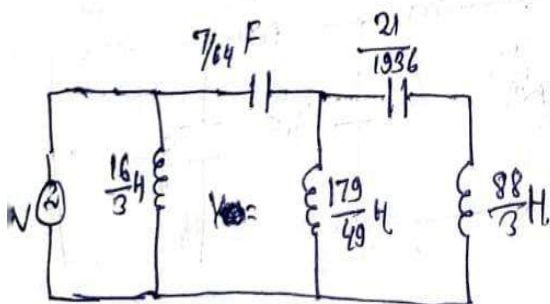
$$\begin{array}{l} \frac{44}{7}s^3 + 2s^5 \overline{) \frac{7}{4}s^2 + \frac{5}{8}s^4} \left(\frac{7}{44s} \times \frac{7}{4} \rightarrow Y(s) \right. \\ \underline{\frac{7}{4}s^2 + \frac{49}{88}s^4} \quad L = \frac{44 \times 4}{2 \times 7} H \end{array}$$



$$\begin{array}{l} \frac{3}{44}s^4 \overline{) \frac{44}{8}s^3 + 2s^5} \left(\frac{44}{3s} \times \frac{44}{7} \rightarrow Z(s) \right. \\ \underline{\frac{44}{8}s^3 + \frac{44}{7}s^5} \end{array}$$

$$\begin{array}{l} C = \frac{3 \times 7}{44 \times 44} F \quad \frac{44}{7}s^3 \\ \underline{2s^5} \overline{) \frac{3}{44}s^4} \left(\frac{1}{2s} \times \frac{3}{44} \rightarrow Y(s) \right. \\ \underline{\frac{3}{44}s^4} \end{array}$$

Question 3. Determine the foster I for the given Impedance.

Que 3 $Z(s) = \frac{5(s+1)(s+4)}{(s+3)(s+5)} = \frac{A}{(s+3)} + \frac{B}{s+5} + \frac{C}{s}$

Foster-I

$$A = \frac{5 \times (-2) \times (1)}{(2)} = -\frac{10}{2} = -5 \quad (\text{Negative})$$




$$\frac{Z(s)}{s} = \frac{5(s+1)(s+4)}{s(s+3)(s+5)} = \frac{A}{(s+3)} + \frac{B}{(s+5)} + \frac{C}{s}$$

$$A = \frac{5 \times (-2) \times (1)}{2 \times (-3)} = \frac{10}{6} = \frac{5}{3}$$

$$B = \frac{5 \times (-4) \times (-1)}{(-2) \times (-5)} = \frac{20}{10} = 2$$

$$C = \frac{5 \times 1 \times 4}{3 \times 5} = \frac{20}{15} = \frac{4}{3}$$
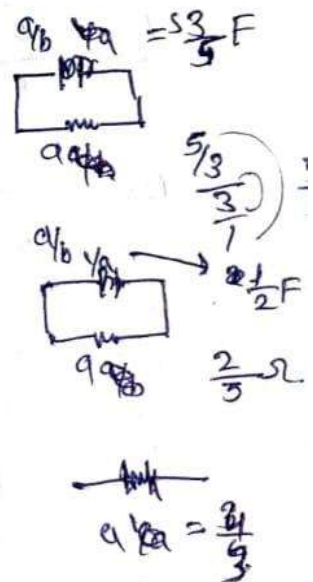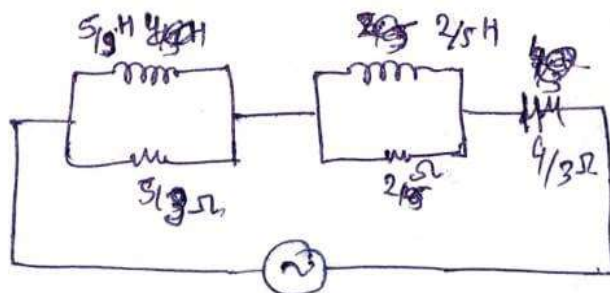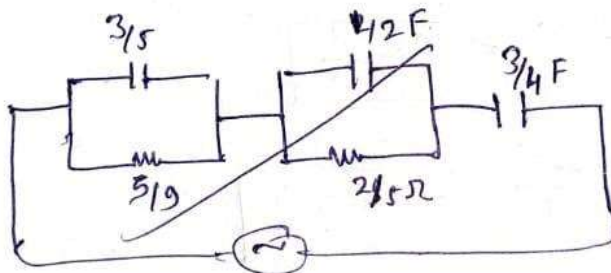
$$Z(s) = \frac{5 \times 5/3}{s+3} + \frac{5 \times 2}{(s+5)} + \frac{5 \times 4/3}{s}$$



Question 4 calculate the Cauer I for given Impedance.

Que 4 $Z(s) = \frac{(s+8)(s+4)}{(s+2)(s+6)} = \frac{s^2 + 4s + 8s + 32}{s^2 + 2s + 6s + 12} = \frac{s^2 + 12s + 32}{s^2 + 8s + 12}$

Lauer-I

$Z(s) = \frac{s^2 + 12s + 32}{s^2 + 8s + 12}$ $Y(s) = \frac{s^2 + 8s}{s^2 + 8s + 12}$

$$\begin{array}{r} s^2 + 12s + 32 \overline{) s^2 + 8s + 12} \\ \underline{s^2 + 8s + 12} \\ -4s + 20 \end{array} \quad \begin{array}{r} s^2 + 8s + 12 \overline{) s^2 + 12s + 32} \\ \underline{s^2 + 8s + 12} \\ 4s + 20 \end{array}$$


$s^2 + 8s + 12 \overline{) s^2 + 12s + 32} \rightarrow Z(s) \quad 1\Omega$

$4s + 20 \overline{) s^2 + 8s + 12} \left[\frac{1}{4} Y(s) \quad C = \frac{1}{4} F \right]$

$3s + 12 \overline{) 4s + 20} \left[\frac{4}{3} Z(s) \quad \frac{4}{3}\Omega \right]$

$4 \overline{) 3s + 12} \left[\frac{3}{4} Y(s) \quad C = \frac{3}{4} F \right]$

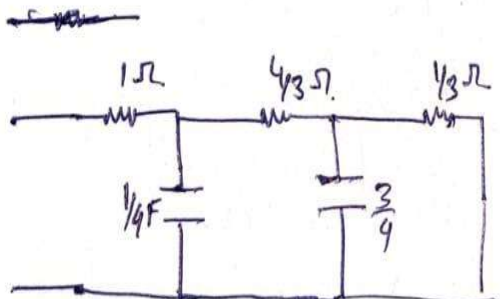
$12 \overline{) 4} \left[\frac{4}{12} Z(s) \quad \frac{1}{3}\Omega \right]$




Verification by Simulation:

Question 1. Determine the foster I and foster II for the given Impedence.

Circuit Diagram:

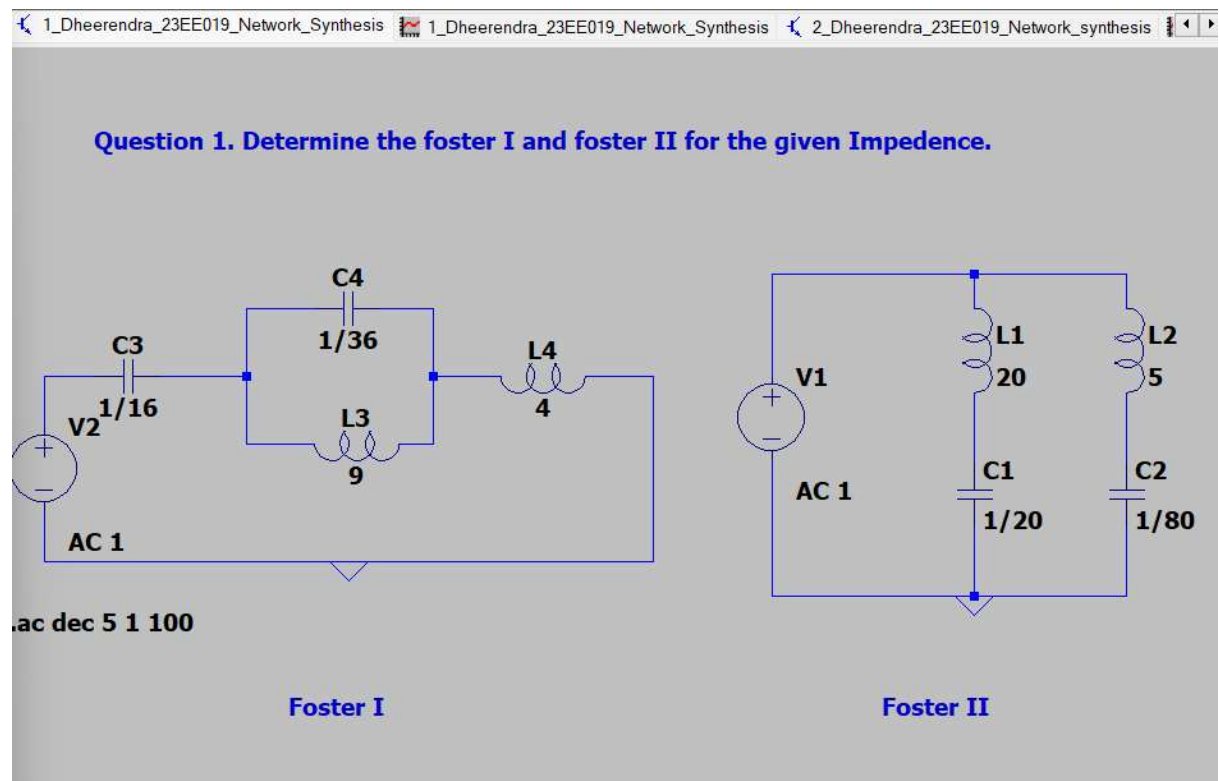


Plot of Voltage/Current:

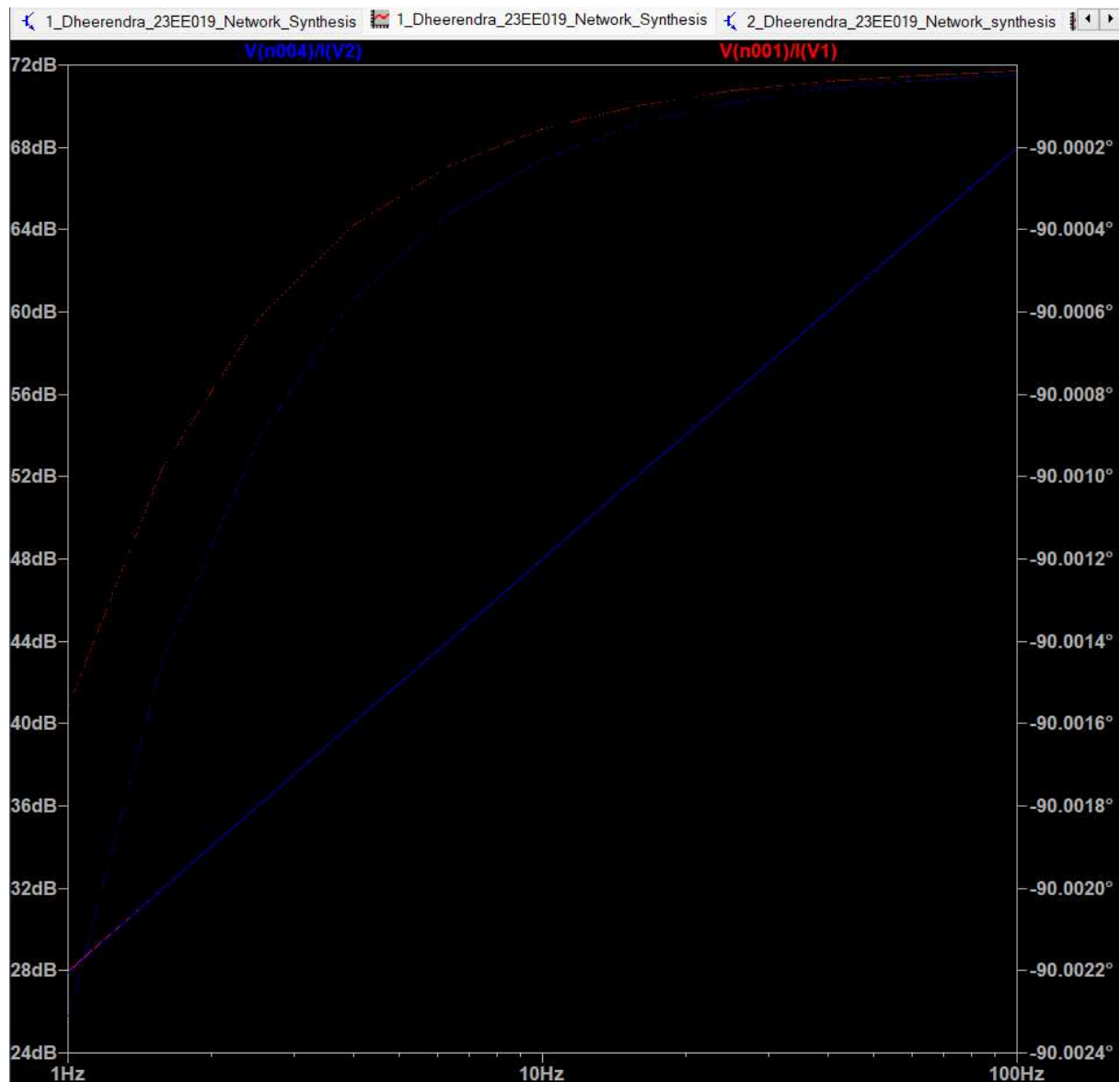

Question 2 calculate the Cauer I and Cauer II.

Circuit Diagram:

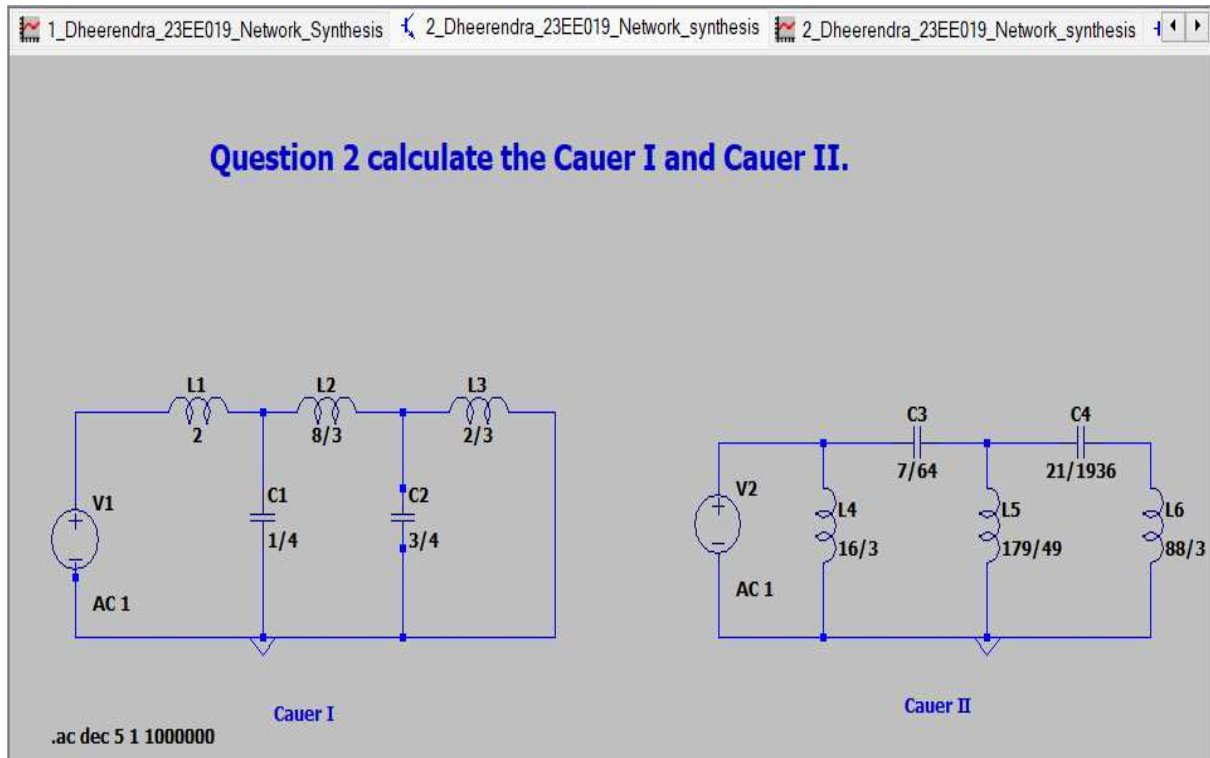


Plot of Voltage/Current:




Question 3. Determine the foster I for the given Impedance.

Circuit Diagram:

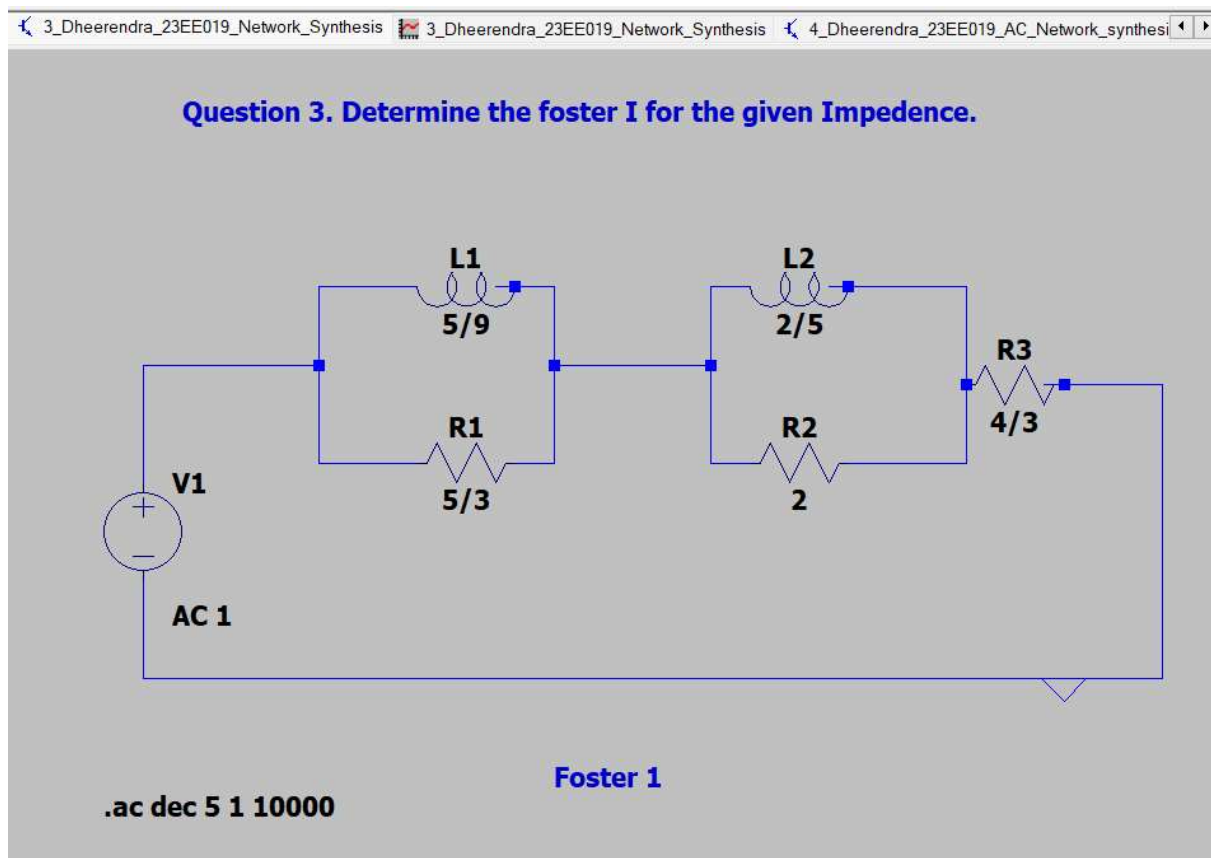


Plot of Voltage/Current:

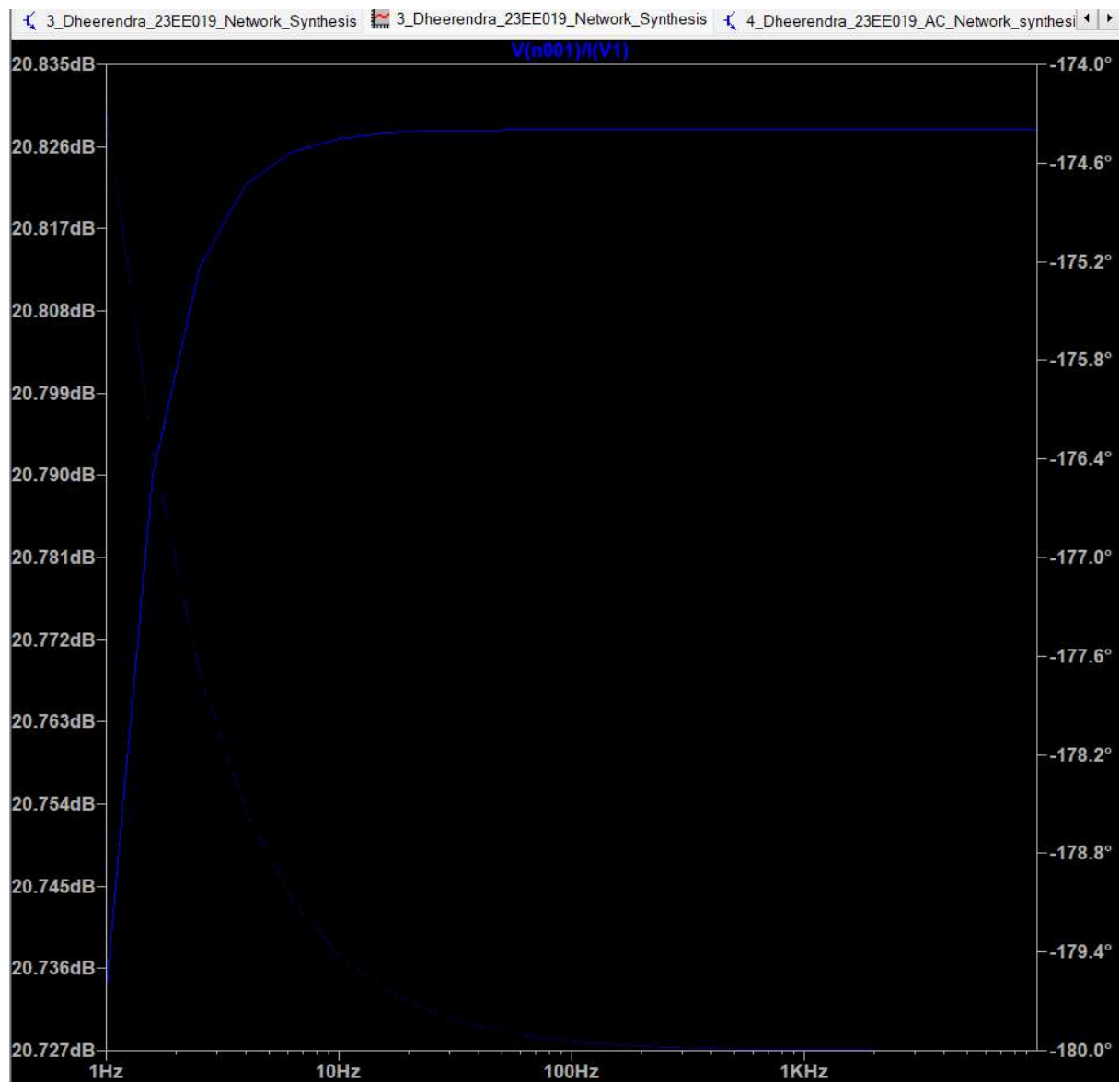


Question 4 calculate the Cauer I for given Impedance.

Circuit Diagram:

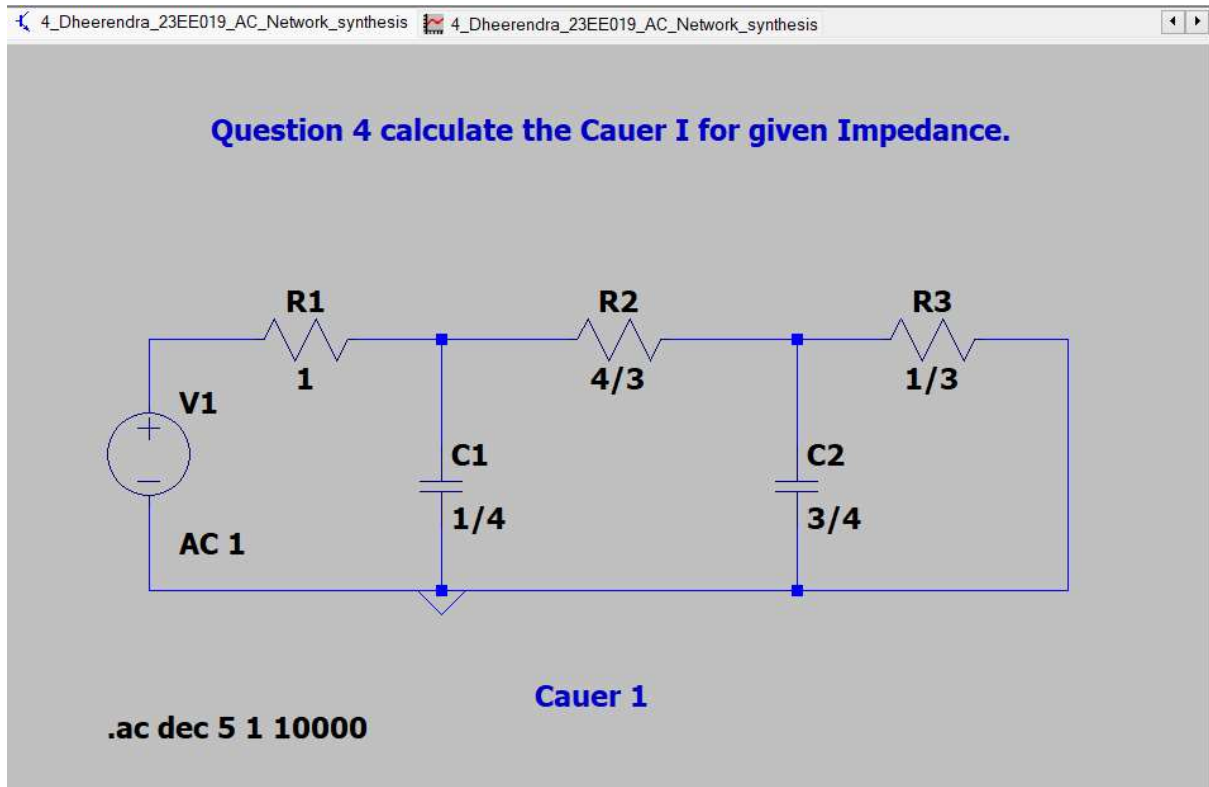

Plot of Voltage/Current:

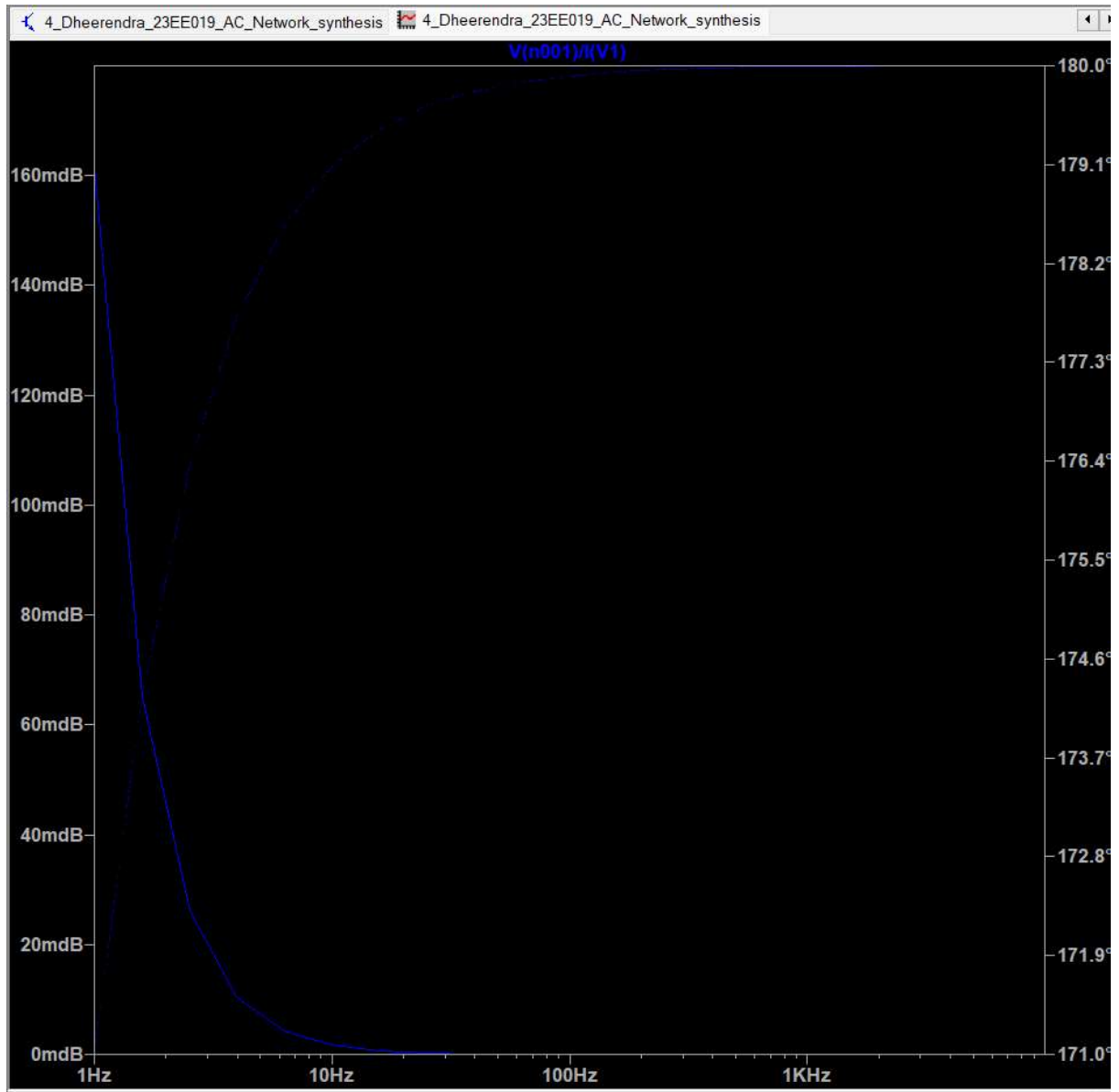

Results and Conclusion:

As we see that the theoretical values are approximately equal to the practical values hence Network synthesis Foster I and Foster II and Cauer I and Cauer II are verified.